

Lab Report 6 MIPS Single-cycle

Owner: Vishal J Parikh.


Part A:

1. A completed version of Table 1.

cycle	reset	pc	instruction	branch	srca	srcb	aluout	zero	pcsrc	write data	mem write	read data
1	1	0	addi \$2,\$0,5	0	0	5	5	0	0	5	0	x
2	0	4	addi \$3, \$0, 12	0	0	c	c	0	0	x	0	x
3	0	8	addi \$7, \$3, -9	0	x	-9	3	0	0	x	0	x
4	0	c	or \$4, \$7, \$2	0	3	5	7	0	0	5	0	x
5	0	10	and \$5, \$3, \$4	0	c	7	4	0	0	7	0	x
6	0	14	add \$5, \$5, \$4	0	4	7	b	0	0	7	0	x
7	0	18	beq \$5, \$7, end	1	b	3	8	0	0	3	0	x
8	0	1c	slt \$4, \$3, \$4	0	c	7	0	0	0	7	0	x
9	0	20	beq \$4 \$0, around	1	0	0	0	1	1	0	0	x
10	0	24	addi \$5 \$0, 0	0								
11	0	28	slt \$4, \$7, \$2	0	3	5	1	0	0	5	0	x
12	0	2c	add \$7, \$4, \$5	0	1	b	c	0	0	b	0	x
13	0	30	sub \$7, \$7, \$2	0	c	5	7	0	0	5	0	x
14	0	34	sw \$7, 68(\$3)	0	38	c	50	0	0	7	1	x
15	0	38	lw \$2,80(\$0)	0	50	0	50	0	0	5	0	7
16	0	3c	j end	1			0	0	0	0	0	x
17	0	40	addi \$2, \$0, 1	0								
18	0	44	sw \$2, 84(\$0)	0	54	0	54	0	0	7	1	x

 2. An image of the simulation waveforms showing correct operation of the unmodified processor.

Does it write the correct value to address 84? : **YES**



```
# Simulation succeeded
# ** Note: $stop : C:/intelFPGA_lite/18.1/ECE 469/mips/mipstest.sv(32)
# Time: 125 ps Iteration: 1 Instance: /mipstest
# Break in Module mipstest at C:/intelFPGA_lite/18.1/ECE 469/mips/mipstest.sv line 32
VSIM 2> run
```

Lab Report 6
MIPS Single-cycle

Part B:

1. List of the new instructions implemented, their encoding, marked up versions of the Datapath schematic and decoder tables that include the new instructions.

BNE -- *Branch on not equal*

Description:	Branches if the two registers are not equal
Operation:	if $S_s \neq S_t$ advance_pc (offset $\ll 2$); else advance_pc (4);
Syntax:	bne S_s, S_t, offset
Encoding:	0001 01ss ssst tttt iiii iiii iiii iiii

ORI -- *Bitwise or immediate*

Description:	Bitwise ors a register and an immediate value and stores the result in a register
Operation:	$S_t = S_s \mid \text{imm}$; advance_pc (4);
Syntax:	ori S_t, S_s, imm
Encoding:	0011 01ss ssst tttt iiii iiii iiii iiii

3. The contents of your memfile2.dat containing your test2 machine language code.

34088000
20098000
350a8001
11090005
0128582a
15600001
08100009
01485022
350800ff
016a5820
01484022
ad680052

Lab Report 6
MIPS Single-cycle

2. Your SystemVerilog code for your modified MIPS with the changes

mips.sv

```
1 // files needed for simulation:
2 // mipsttest.sv mipstop.sv, mipsmem.sv, mips.sv, mipsparts.sv
3
4 // single-cycle MIPS processor
5 module mips(input logic clk, reset,
6             output logic [31:0] pc,
7             input logic [31:0] instr,
8             output logic memwrite,
9             output logic [31:0] aluout, writedata,
10            input logic [31:0] readdata);
11
12     logic memtoreg, branch,
13           pcsrc, zero,
14           regdst, regwrite, jump;
15     logic [1:0] alusrc;
16     logic [2:0] alucontrol;
17
18     controller c(instr[31:26], instr[5:0], zero,
19                 memtoreg, memwrite, pcsrc,
20                 alusrc, regdst, regwrite, jump,
21                 alucontrol);
22     datapath dp(clk, reset, memtoreg, pcsrc,
23                alusrc, regdst, regwrite, jump,
24                alucontrol,
25                zero, pc, instr,
26                aluout, writedata, readdata);
27 endmodule
28
29 module controller(input logic [5:0] op, funct,
30                  input logic zero,
31                  output logic memtoreg, memwrite,
32                  output logic pcsrc,
33                  output logic [1:0] alusrc,
34                  output logic regdst, regwrite,
35                  output logic jump,
36                  output logic [2:0] alucontrol);
37
38     logic [1:0] aluop;
39     logic branch;
40
41     maindec md(op, memtoreg, memwrite, branch,
42               alusrc, regdst, regwrite, jump,
43               aluop);
44     aludec ad(funct, aluop, alucontrol);
```

```
49
50 module maindec(input logic [5:0] op,
51                output logic memtoreg, memwrite,
52                output logic branch,
53                output logic [1:0] alusrc,
54                output logic regdst, regwrite,
55                output logic jump,
56                output logic [1:0] aluop);
57
58 logic [9:0] controls;
59
60 assign {regwrite, regdst, alusrc,
61        branch, memwrite,
62        memtoreg, jump, aluop} = controls;
63
64 always_comb
65 case(op)
66 6'b000000: controls = 10'b1100000010; //Rtype
67 6'b100011: controls = 10'b1001001000; //LW
68 6'b101011: controls = 10'b0001010000; //SW
69 6'b000100: controls = 10'b0000100001; //BEQ
70 6'b000101: controls = 10'b0100100001; //BNE
71 6'b001000: controls = 10'b1001000000; //ADDI
72 6'b001101: controls = 10'b1010000011; //ORI
73 6'b000010: controls = 10'b0000000100; //J
74 default:   controls = 10'bxxxxxxxx; //???
75 endcase
76 endmodule
77
78 module aludec(input logic [5:0] funct,
79               input logic [1:0] aluop,
80               output logic [2:0] alucontrol);
81
82 always_comb
83 case(aluop)
84 2'b00: alucontrol = 3'b010; // add
85 2'b01: alucontrol = 3'b110; // sub
86 2'b11: alucontrol = 3'b001; // OR
87 default: case(funct) // RTYPE
88 6'b100000: alucontrol = 3'b010; // ADD
89 6'b100010: alucontrol = 3'b110; // SUB
90 6'b100100: alucontrol = 3'b000; // AND
91 6'b100101: alucontrol = 3'b001; // OR
92 6'b101010: alucontrol = 3'b111; // SLT
```

Lab Report 6
MIPS Single-cycle

```

95 endmodule
96
97 module datapath(input logic clk, reset,
98               input logic memtoreg, pccsrc, regdst,
99               input logic [1:0] alusrc,
100              input logic regwrite, jump,
101              input logic [2:0] alucontrol,
102              output logic zero,
103              output logic [31:0] pc,
104              input logic [31:0] instr,
105              output logic [31:0] aluout, writedata,
106              input logic [31:0] readdata);
107
108 logic [4:0] writereg;
109 logic [31:0] pcnext, pcnextbr, pcplus4, pcbranch;
110 logic [31:0] signimm, signimmsh, zeroimm;
111 logic [31:0] srca, srcb;
112 logic [31:0] result;
113
114 // next PC logic
115 flopr #(32) pcreg(clk, reset, pcnext, pc);
116 adder      pcadd1(pc, 32'b100, pcplus4);
117 s12       immsh(signimm, signimmsh);
118 adder      pcadd2(pcplus4, signimmsh, pcbranch);
119 mux2 #(32) pcbrmux(pcplus4, pcbranch, pccsrc, pcnextbr);
120 mux2 #(32) pcmux(pcnextbr, {pcplus4[31:28], instr[25:0], 2'b00},
121               jump, pcnext);
122
123 // register file logic
124 regfile rf(clk, regwrite, instr[25:21],
125           instr[20:16], writereg,
126           result, srca, writedata);
127 mux2 #(5) wrmux(instr[20:16], instr[15:11], regdst, writereg);
128 mux2 #(32) resmux(aluout, readdata, memtoreg, result);
129 signext    se(instr[15:0], signimm);
130 zeroext    ze(instr[15:0], zeroimm);
131
132 // ALU logic
133 mux4to1    srcbmux(writedata, signimm, zeroimm, alusrc, srcb);
134 alu        alu(.A(srca), .B(srcb), .F(alucontrol), .Y(aluout), .zero(
135 endmodule
136

```

mipsparts.sv

```

32 module zeroext(input logic [15:0] a,
33               output logic [31:0] y);
34
35     assign y = {16'b0, a};
36 endmodule
37
38 module signext(input logic [15:0] a,
39               output logic [31:0] y);
40
41     assign y = {{16{a[15]}}, a};
42 endmodule
43

```

Lab Report 6
MIPS Single-cycle


```
72 module mux4to1(  
73     input logic [31:0] A, B, C,  
74     input logic [1:0] s,  
75     output logic [31:0] Y);  
76  
77     always_comb  
78     case(s)  
79         2'b00: Y = A;  
80         2'b01: Y = B;  
81         2'b10: Y = C;  
82         default: Y = 32'bx;  
83     endcase  
84 endmodule  
85
```

mipstest.sv

```
1 // Example testbench for MIPS processor  
2  
3 module mipstest();  
4  
5     logic        clk;  
6     logic        reset;  
7  
8     logic [31:0] writedata, dataadr;  
9     logic        memwrite;  
10  
11     // instantiate device to be tested  
12     mipstop dut(clk, reset, writedata, dataadr, memwrite);  
13  
14     // initialize test  
15     initial  
16     begin  
17         reset <= 1; # 22; reset <= 0;  
18     end  
19  
20     // generate clock to sequence tests  
21     always  
22     begin  
23         clk <= 1; # 5; clk <= 0; # 5;  
24     end  
25  
26     // check that 7 gets written to address 84  
27     always@(negedge clk)  
28     begin  
29         if(memwrite) begin  
30             if(dataadr === 84 & writedata === -33022) begin  
31                 $display("Simulation succeeded");  
32                 $stop;  
33             end else if (dataadr !== 82) begin  
34                 $display("Simulation failed");  
35                 $stop;  
36             end  
37         end  
38     end  
39 endmodule  
40
```

Lab Report 6 MIPS Single-cycle

5. Simulation waveforms Part B

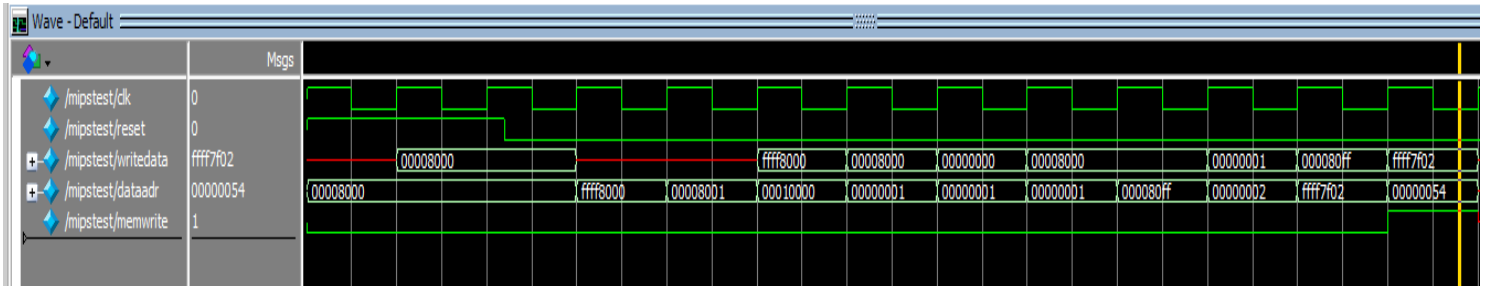

```
#
# add wave *
# view structure
# .main_pane.structure.interior.cs.body.struct
# view signals
# .main_pane.objects.interior.cs.body.tree
# run -all
# Simulation succeeded
# ** Note: $stop : C:/intelFPGA_lite/18.1/ECE 469/mips/mipstest.sv(32)
# Time: 125 ps Iteration: 1 Instance: /mipstest
# Break in Module mipstest at C:/intelFPGA_lite/18.1/ECE 469/mips/mipstest.sv line 32
VSIM 2> run
```

Extended functionality. Main Decoder:

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}	Jump			
R-type	000000	1	1	0	0	0	0	10	0			
lw	100011	1	0	1	0	0	1	00	0			
sw	101011	0	X	1	0	1	X	00	0			
beq	000100	0	X	0	1	0	X	01	0			
addi	001000	1	0	1	0	0	0	00	0			
j	000010	0	X	X	X	0	X	XX	1			
ori	001101	1	0	1	0	0	0	11	0			
bne	000101	0	1	0	1	0	X	01	0			


Extended functionality. ALU Decoder:

ALUOp _{1:0}	Meaning
00	Add
01	Subtract
10	Look at funct field
11	ori

Lab Report 6 MIPS Single-cycle


Overall:

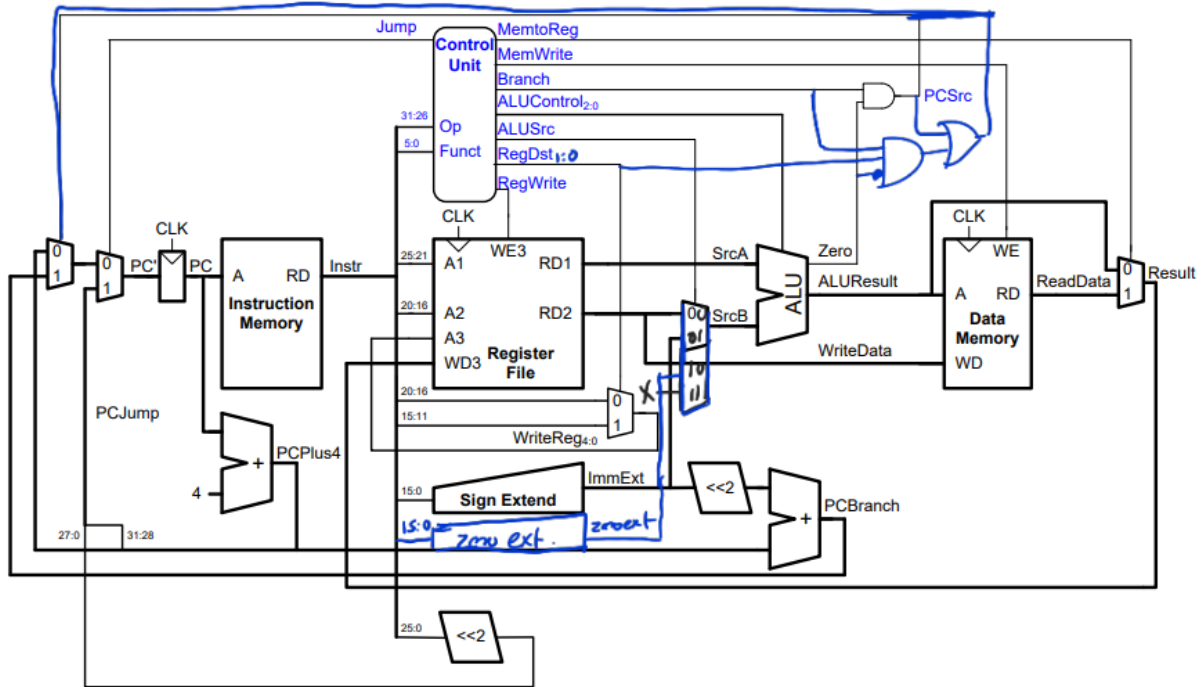1. RTL view from Quartus' compilation result of your MIPS processor: before and after the modification. Identify and highlight the changes of your modification parts.





Single-cycle MIPS processor

Mipstop


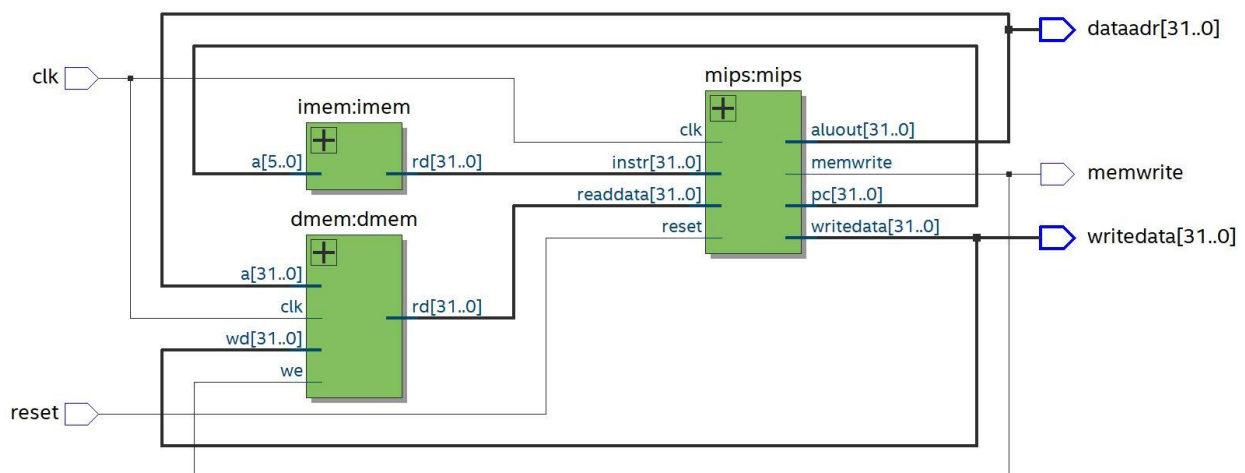


Lab Report 6 MIPS Single-cycle

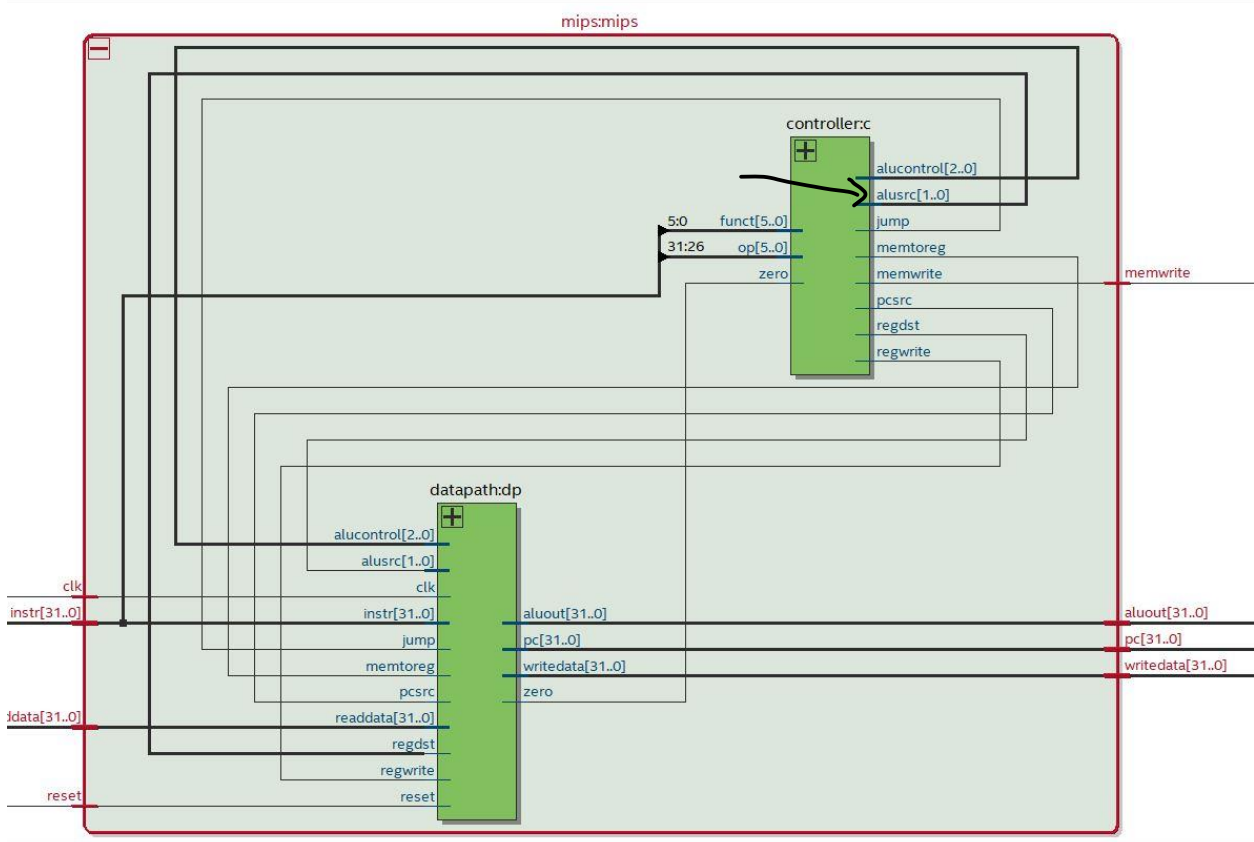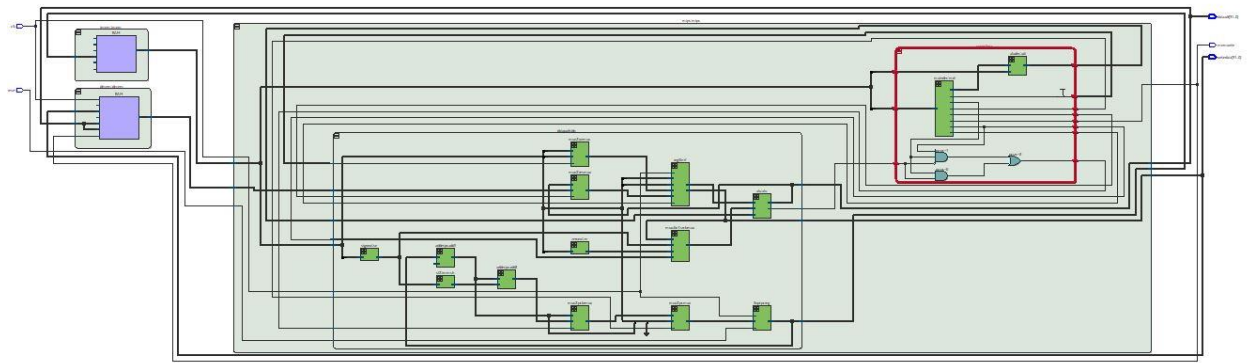




Lab Report 6 MIPS Single-cycle

Controller

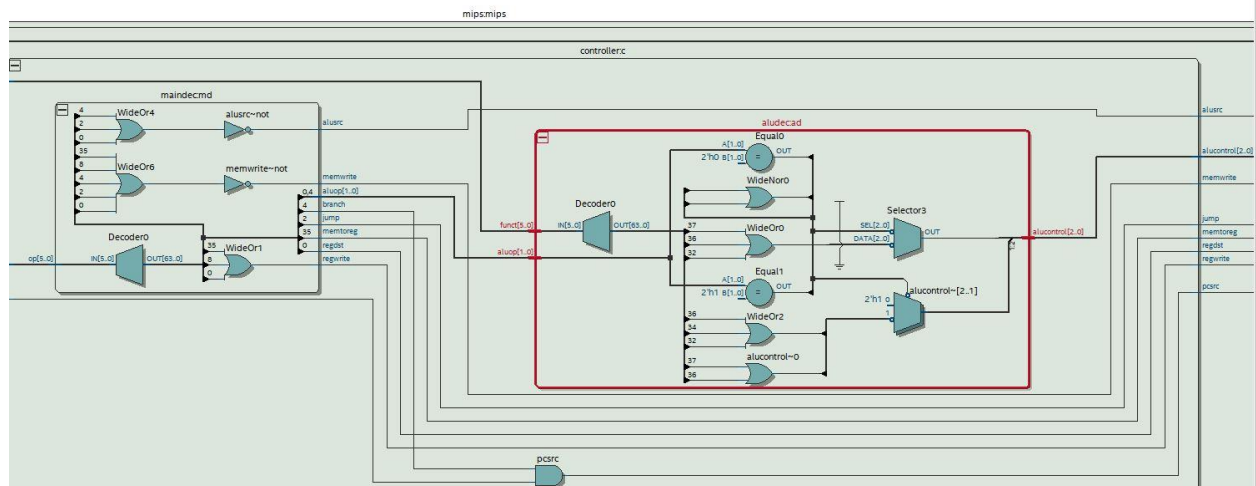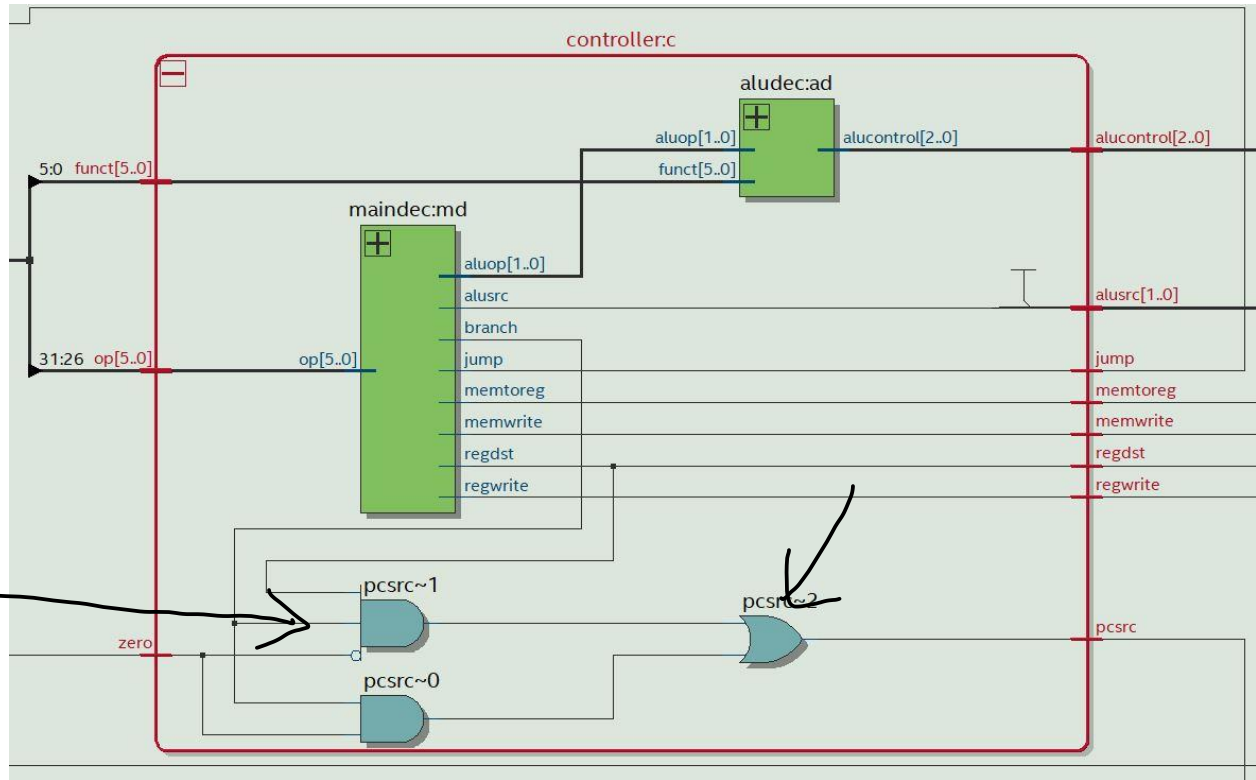

Lab Report 6 MIPS Single-cycle

Datapath

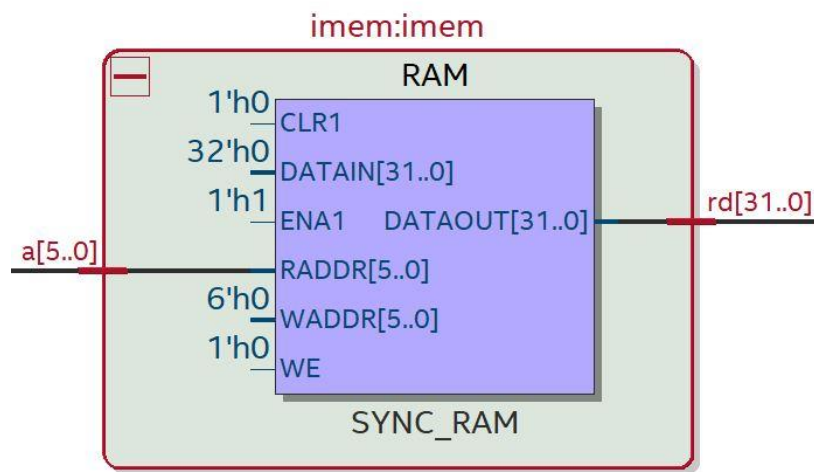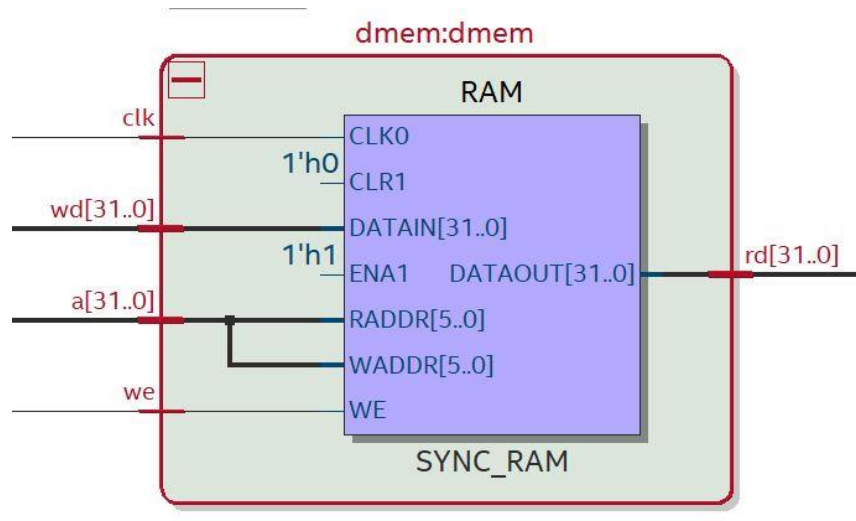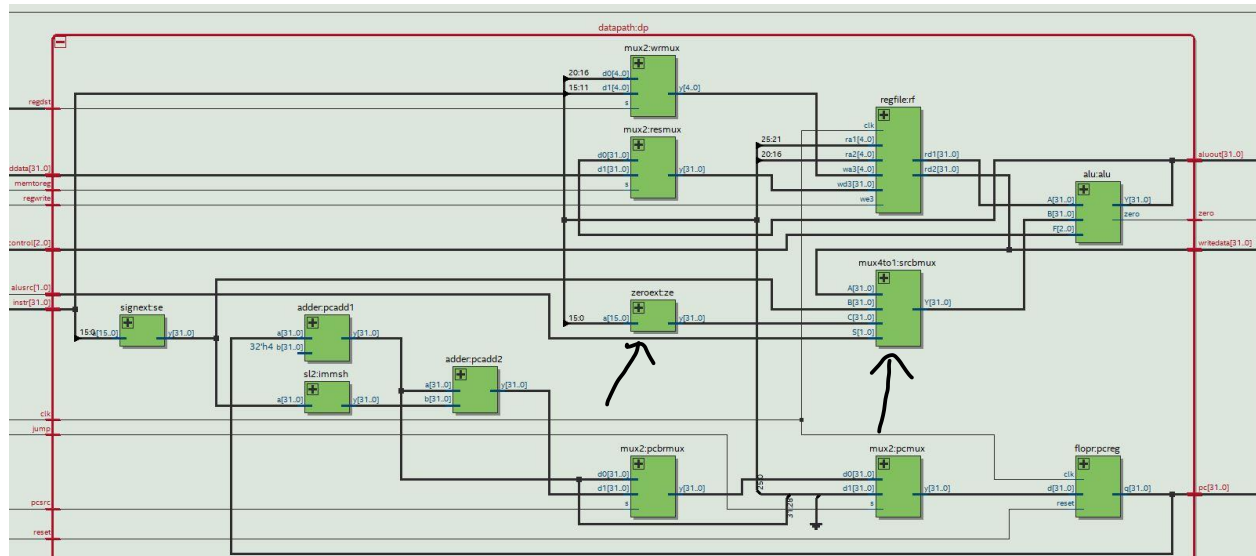

Lab Report 6
MIPS Single-cycle

2. Workload report:

How many hours have you spent for this lab?

- More than a week (avg 4 hours every day during this time)

Which activity takes the most significant amount of time? This will not affect your grade (unless omitted).

- Figuring out the code, connections other than logic part was fine.